



Table of Contents

Preface	v
Introduction	1
Cabling:	1
Hubs	2
Resource Links	2
1 Basics	5
1.1 Information Transfer and Power Supply	5
1.2 Electrical Circuit	7
1.2.1 Blown Circuits	7
1.2.2 Committed Circuits	7
1.2.3 Issues in Homes without Dedicated Circuits	7

1.3	1.2.4 The Works of an Electrical Circuit	8
	Electrical Quantities	9
	1.3.1 What is an Electrical Current?	9
	1.3.2 Ohm's Law	13
	1.3.3 Fundamental Laws of Electronics	14
	1.3.4 Kirchhoff's Laws	15
	1.3.5 Work, Performance and Efficiency	16
1.4	Series Connection	18
1.5	Parallel Connection	20
1.6	Adaptation	24
	1.6.1 Transmitting Voltages, Amperages and Resistance Values	25
	1.6.2 Deciding Transmitter Power Dissipation	27
1.7	Fork Connection	32
	1.7.1 Operating Voltage Supply	33
	1.7.2 DC, AC and Mixed Voltages	36
1.8	Sinusoidal and Non-sinusoidal Tensions	41
1.9	Building Blocks for Signal Processing	45
	1.9.1 Kinds of Audio Signal Processors	46
	1.9.2 Brief Explanation of Digital Signal Processing, Compression, Encryption, and File Translation	47
1.10	Capacitor	50
	1.10.1 Coil	52
	1.10.2 Low Pass, High Pass and Band Pass	54
	1.10.3 Resonance Circuits	56
1.11	Band Filter	58
1.12	Transistor	63
1.13	Op AMP	65
	1.13.1 Voltage	66
	1.13.2 Amperage	66
	1.13.3 Watts	66
	1.13.4 Operation Amp Specifications	67
1.14	Optoelectronics	69
	1.14.1 General Information about Optoelectronics	69
	1.14.2 Uses of Optoelectronics Devices	73
	1.14.3 Receiver Components	74
	1.14.4 Emitter Components	75

1.15	Installation of Electrical Resources	77
1.15.1	Generation and Distribution of Electrical Energy	81
1.15.2	Documents for the Electrical Energy	86
1.15.3	Most Effective Method to Use less Electricity	91
1.15.4	Protective Measures	92
1.15.5	Dimensioning of Cables and Fuses	96
1.15.6	Checking Protective Measures	97
1.15.7	Project: Installation of a Power Supply for 24PCs	98
2	Digital Technology	103
2.1	Introduction	103
2.2	Combinatorial Elements	105
2.2.1	Essential Combinatorics Rules	105
2.2.2	AND Element	106
2.2.3	OR Element	108
2.2.4	NOT Element	111
2.2.5	NAND Element (NOT-AND)	113
2.2.6	NOR Element (NOT-OR)	114
2.3	Switching Algebra	115
2.3.1	AND Operation	115
2.3.2	OR Operation	115
2.3.3	NOT Operation	115
2.3.4	Some Basic Laws for Boolean Algebra	116
2.3.5	Calculation Rules	116
2.3.6	Law of De Morgan	117
2.3.7	Application Examples	118
2.4	Number Systems	120
2.4.1	Decimal system	124
2.4.2	Dual system	125
2.4.3	Spot Worth Guidelines in Binary Number System	126
2.4.4	Octal and Hexadecimal System	130
2.4.5	Conversion: Decimal Numbers in Binary Numbers	132
2.4.6	Computing with Binary Numbers	135
2.5	Binary Codes	137

2.5.1	BCD Code (BCD: Binary Coded Decimal Digit)	139
2.5.2	Weighted Codes	141
2.5.3	Unweighted Codes	142
2.5.4	Error-detecting Codes	144
2.6	Basic Switching Networks	144
2.6.1	Adder	146
2.6.2	Arithmetic Logic Unit (ALU)	148
2.6.3	Equivalence Element	150
2.6.4	Pseudotetradic Recognizer	151
2.6.5	Number Comparator	153
2.6.6	Bus Driver, 3-State Driver	154
2.7	Encoder	156
2.7.1	Decimal BCD (8421) Encoder	158
2.7.2	BCD (8421) Decimal Encoder	158
2.7.3	Binary Gray Encoder	160
2.8	Multiplexer, Demultiplexer	161
2.8.1	Multiplexer (MUX)	163
2.8.2	Demultiplexer (DMUX)	168
2.9	Bistable Elements, Flip-flops	169
2.9.1	Successive Circuit	169
2.9.2	RS Flip-flop	171
2.9.3	D Flip-flop	175
2.9.4	Single-edge Flip-flops	177
2.9.5	Conversion of Flip-flops	177
2.9.6	Two-Memory Flip-flop (Master-Slave Flip-flop)	178
2.9.7	Transcoder	179
2.10	Counting Circuits	181
2.10.1	Asynchronous Counter	182
2.10.2	Synchronous Counters	183
2.10.3	Integrated Counting Circuits	185
2.11	Registers	186
2.11.1	Shift Register	186
2.11.2	Parallel-to-serial Converter	188
2.11.3	Serial-to-Parallel Converter	189
2.11.4	Scrambler, Descrambler	190
2.11.5	Latch	191

2.12	Arithmetic Units	192
2.12.1	Serial Adder	194
2.12.2	Serial Subtractor	195
2.12.3	Serial Multiplier	195
2.12.4	Parallel Adder	196
2.13	Digital-to-analog Converter	197
2.13.1	DA Converter with Stepped Resistors	199
2.13.2	DA Converter with Resistance Ladder / R2R Network	200
2.14	Analog-to-digital Converter	202
2.14.1	AD Converter with Resistor Network	203
2.14.2	AD Converter after the Sawtooth Method	204
2.14.3	AD Converter after the Weighing Process	205
2.14.4	AD Converter According to the Parallel Method	206
2.14.5	AD Conversion by Delta Modulation	208
2.15	Semiconductor Memory	208
2.15.1	Read-only Memory	210
2.15.2	Read Write Memory	211
2.16	Computer Architecture	212
2.16.1	Von Neumann Architecture	213
2.16.2	Harvard Architecture	215
2.16.3	Microcontroller Architecture	216
3	Workstations	220
3.1	Introduction	220
3.2	General	222
3.2.1	Networking Possibilities	223
3.2.2	Structure of a Workstation	225
3.3	PC Case Forms	226
3.3.1	Stationary Devices	227
3.3.2	Mobile Devices	229
3.4	Structure of a Workstation	231
3.4.1	Microprocessor (CPU)	235
3.4.2	Motherboard (Motherboard, Motherboard)	237
3.4.3	Characteristics	241
3.4.4	Chipset	242

3.4.5	Memory	244
3.4.6	Internal Bus Systems	245
3.5	Input and Output	247
3.5.1	Keyboard	250
3.5.2	Mouse	252
3.5.3	Touchpad	253
3.5.4	TrackPoint	254
3.5.5	Peripheral Interfaces	255
3.5.6	Graphics Cards	257
3.5.7	Monitors	258
3.5.8	Possibilities of Input-output Communication	260
3.6	Mass Storage	261
3.6.1	Hard Disks	263
3.6.2	Partitioning and Formatting	264
3.6.3	Hard Disk Connections	266
3.6.4	RAID Systems	267
3.6.5	Optical Recording Systems	269
Index		273